

CS 270: Computer Organization

Logic Design

Instructor:

Professor Stephen P. Carl

Overview of Logic Design


Fundamental Hardware Requirements

- Communication - how to get values from one place to another
- Computation
- Storage

Bits are Our Friends


- Everything is expressed in terms of values 0 and 1
- Communication: low or high voltage on a wire
- Computation: compute fundamental Boolean functions
- Storage: Store bits of information

Digital Signals

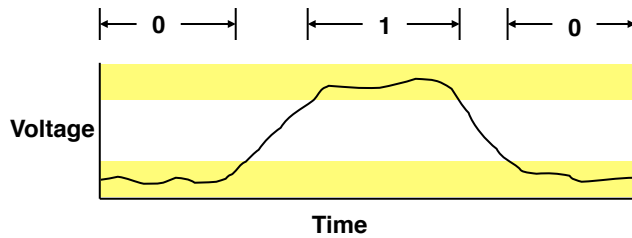


- Use voltage thresholds to extract discrete values from continuous signal
- Simplest version: 1-bit signal
 - Either high range (1) or low range (0)
 - With guard range between them
- Not strongly affected by noise or low quality circuit elements
 - Can make circuits simple, small, and fast


Computing with Logic Gates

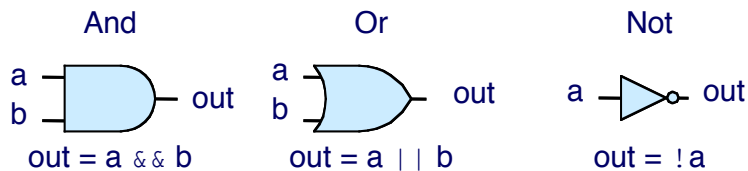

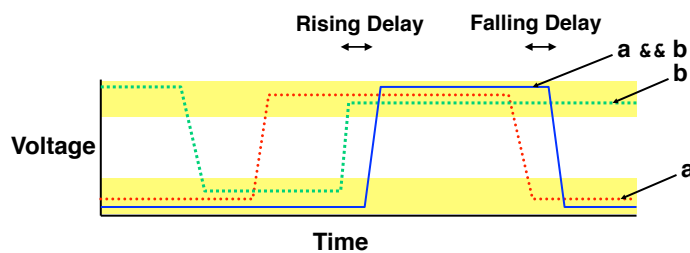- Gate outputs are Boolean functions of inputs - thanks, Claude Shannon!
- Gates respond continuously to changes in inputs
(With some, small delay)




Combinational Circuits

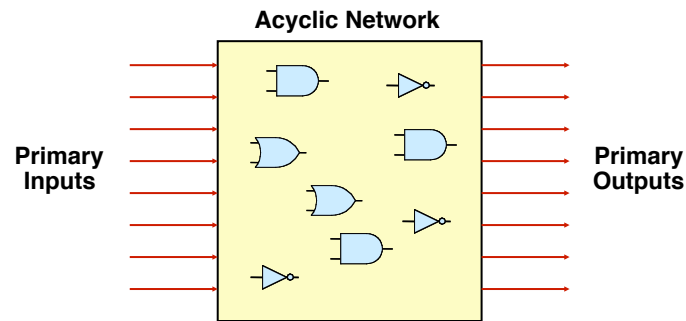

A combinational circuit is an acyclic network of logic gates

- Outputs continuously respond to changes on primary inputs
- After some delay, the primary outputs become Boolean functions of primary inputs

Bit Equality

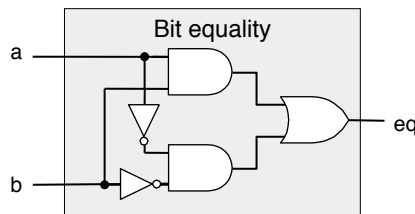

HCL Expression:


```
bool eq = (a&&b) || (!a&&!b)
```

This circuit generates a 1 as output if **a** and **b** are equal, 0 otherwise


Book introduces Hardware Control Language (HCL)

- Very simple hardware description language, in which boolean operations have syntax similar to C logical operations
- You should be able to read it, but we won't write it
- Used to describe control logic for processors

Word Equality

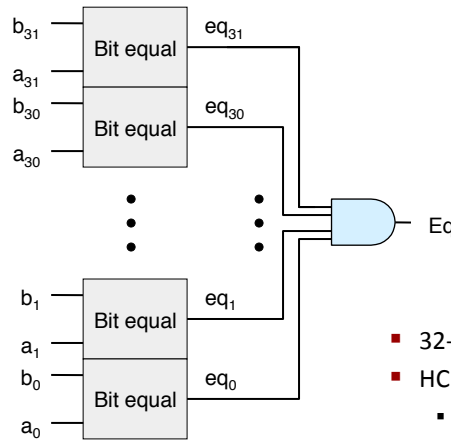

Word-Level Representation

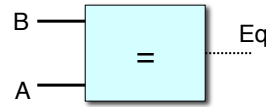


HCL Representation

`bool Eq = (A == B)`

- 32-bit word size
- HCL representation
 - Equality operation
 - Generates Boolean value

Bit-Level Multiplexor

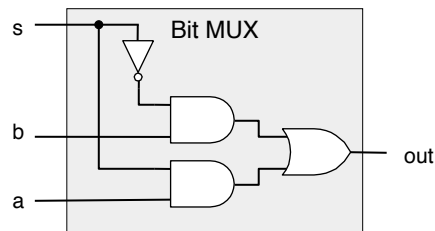


HCL Expression


`bool out = (s&&a) || (!s&&b)`

- *S* is the *control signal*
- *a* and *b* are *data signals*
- Multiplexor outputs *a* when *s*=1, *b* when *s*=0

Word Multiplexor

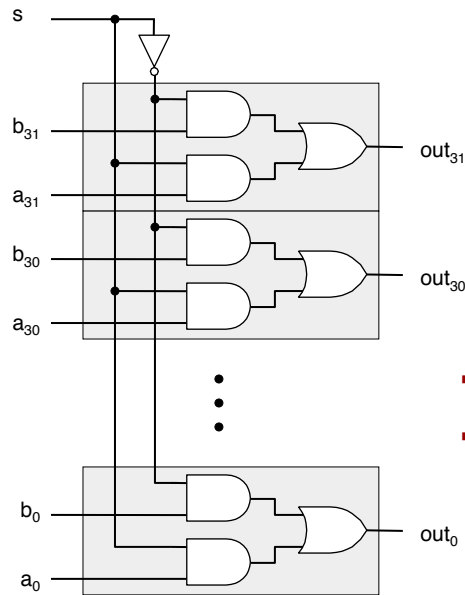

Word-Level Representation

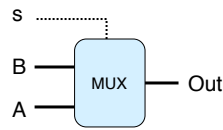


HCL Representation

```
int Out = [
  s : A;
  1 : B;
];
```

- Select input word A or B depending on control signal s
- HCL representation
 - Case expression
 - Series of test:value pairs
 - Output value for first successful test


Arithmetic Logic Unit

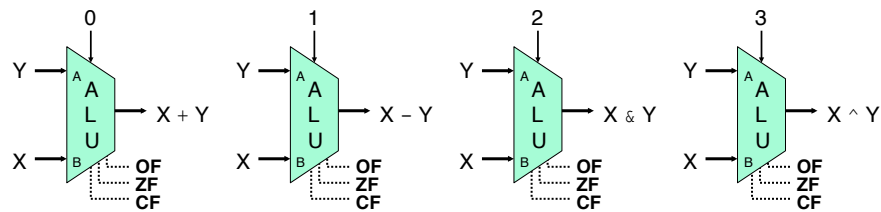


- ALU is made up of Combinational logic
(recall: such logic continuously responds to inputs)
- Control signal selects function computed
(this corresponds to the 4 arithmetic/logical operations in Y86)
- Also computes values for condition codes

Storing and Accessing 1 Bit


Bistable Element

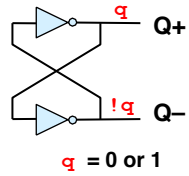


R-S Latch

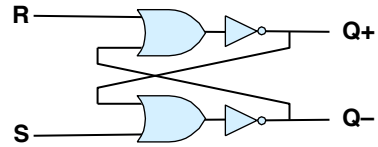


Resetting

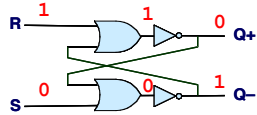

Setting

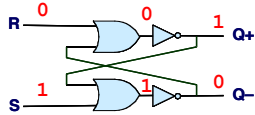


Storing

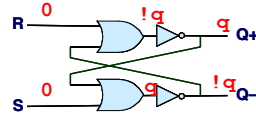


1-Bit Latch


D Latch

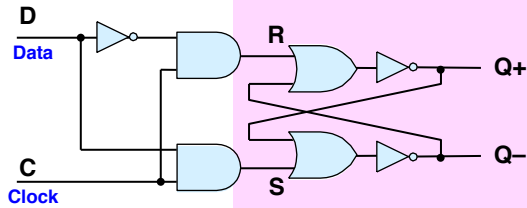


Latching

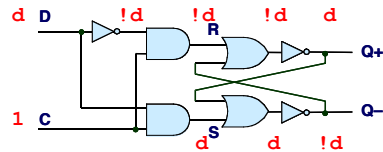

Storing

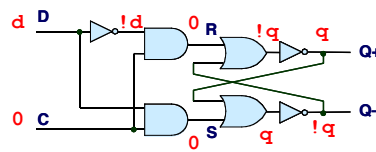


Registers

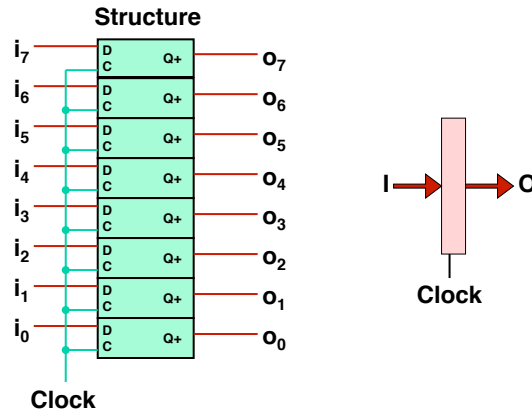


- A *register* stores a word of data
(note: this is different from *program registers* seen in assembly code)
- Collection of latches
- Loads input on rising edge of clock

Register Operation

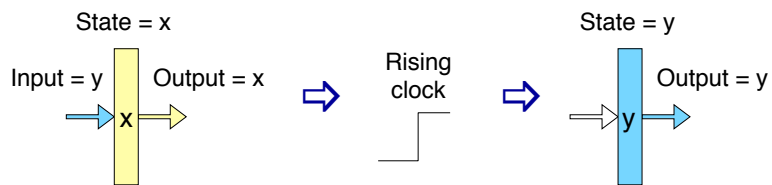

- Stores data bits
- For most of time acts as barrier between input and output
- As clock rises, loads input

Random-Access Memory

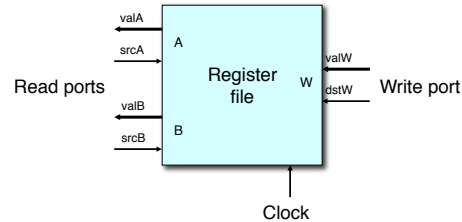

- Stores multiple words of memory
 - Address input specifies which word to read or write
- Register file
 - Holds values of program registers
 - `%eax`, `%esp`, etc.
 - Register identifier serves as address
- Multiple Ports
 - Can read and/or write multiple words in one cycle
 - Each has separate address and data input/output

Summary

- **Computation**
 - Performed by combinational logic
 - Computes Boolean functions
 - Continuously reacts to input changes
- **Storage**
 - Registers
 - Hold single words
 - Loaded as clock rises
 - Random-access memories
 - Hold multiple words
 - Possible multiple read or write ports
 - Read word when address input changes
 - Write word as clock rises